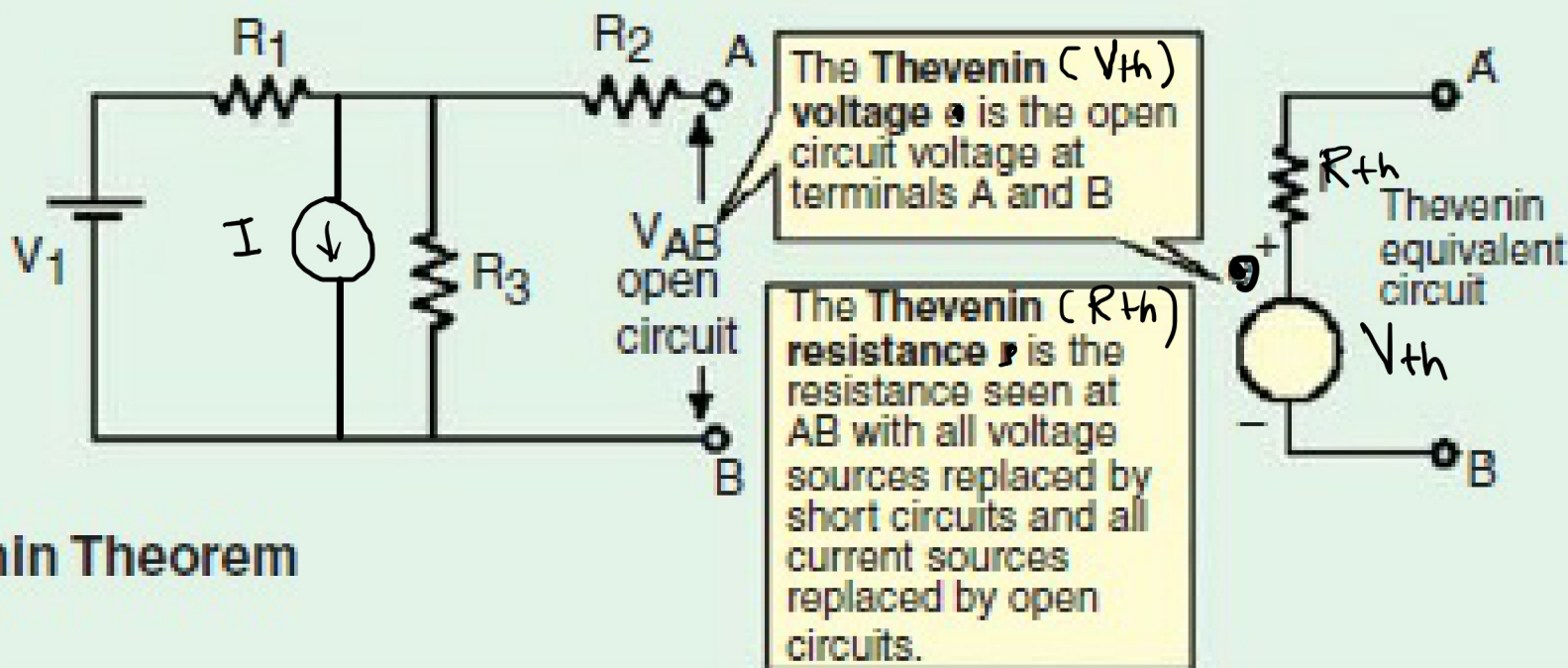


# Thevenin's Theorem

## Statement:


Any linear, active bilateral network can be replaced by a voltage source ( $V_{th}$ ) in series with a resistance ( $R_{th}$ ) where  $V_{th}$  is the open-circuit voltage (i.e. voltage across the two terminals when  $R_L$  is removed) and  $R_{th}$  is the internal resistance of the network as viewed back into the open-circuited network from terminals A and B with all energy sources replaced by their internal resistance. (Ideal current sources by infinite resistance and Ideal voltage source by zero resistance).




# Thevenin's Theorem

Steps to analyse network using Thevenin's Theorem

Given network

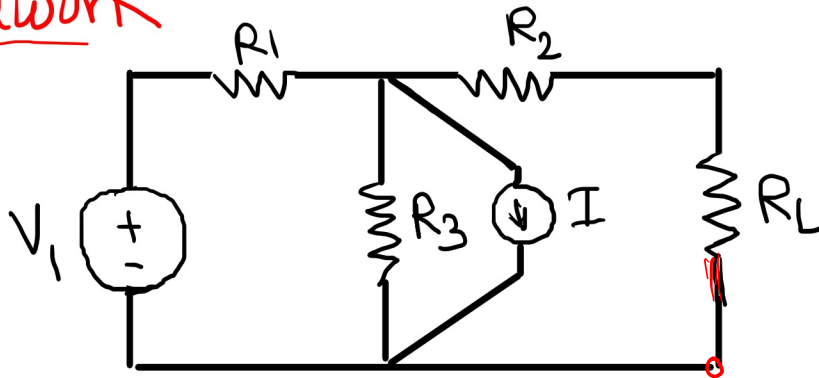


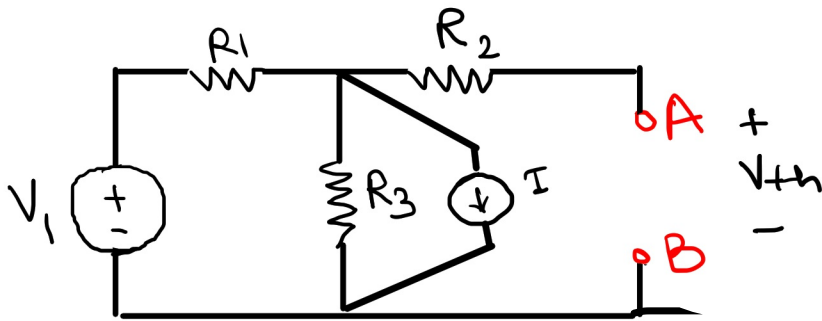1. Remove load resistance  $R_L$  from the given network




2. Find  $V_{th}$  i.e. the open circuit voltage between the terminals (A-B) from where the load is removed using any suitable method (mesh, nodal, source transformation etc..)

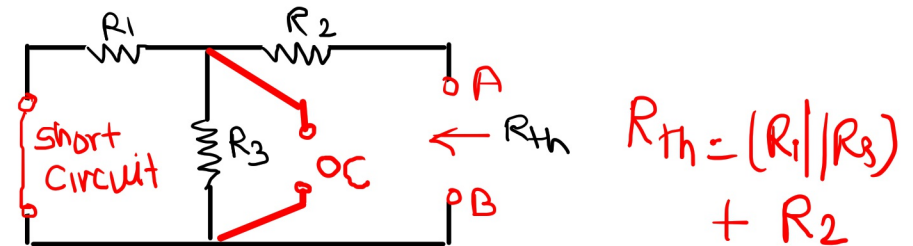
3. Find  $R_{th}$  i.e. resistance looking back into the network from the terminals (A-B) from where the load is removed and energy sources replaced by their internal resistances.




4. Draw thevenin's equivalent circuit

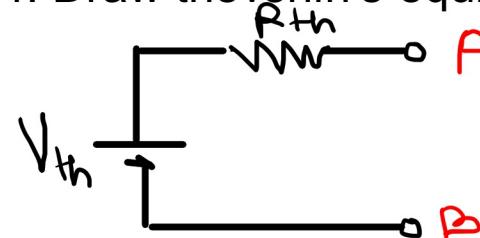

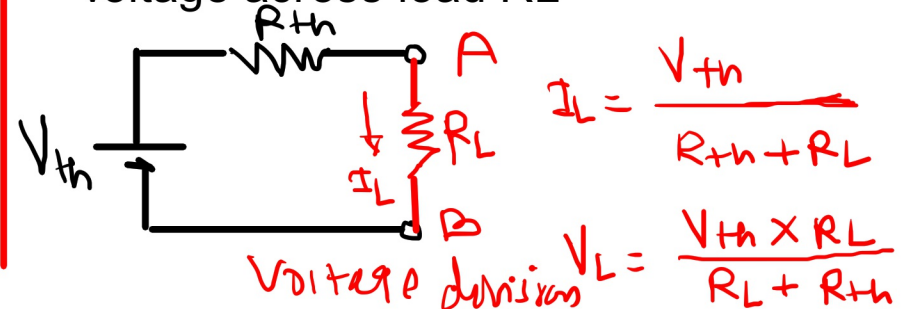5. Connect the load  $R_L$  and find current/voltage across load  $R_L$


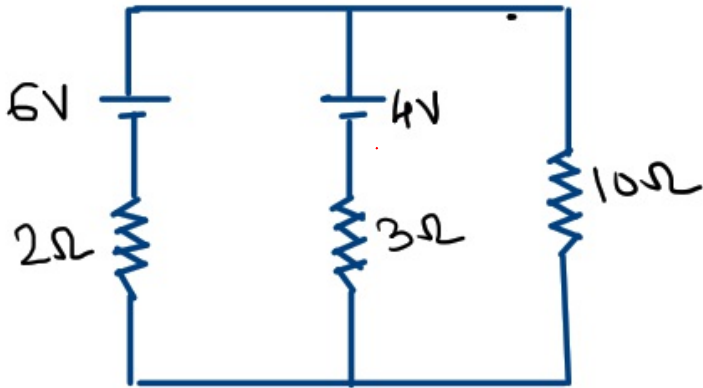
# Example:1 Find current through 10 Ohm resistor using Thevenin's Theorem



②

Find  $V_{th}$   
using KVL

$$V_{th} - 4 - 3I = 0$$

KVL to loop to find  $I$

$$6 - 4 - 3I - 2I = 0$$

$$5I = 2$$

$$I = \frac{2}{5} = 0.4A$$

$$V_{th} = 4 + 3I = 4 + 3 \times 0.4$$

$$V_{th} = 5.2V$$

OR

using Nodal

KCL at node (A)

$$\frac{V-6}{2} + \frac{V-4}{3} = 0$$

$$\frac{3V-18}{6} + \frac{2V-8}{3} = 0$$

$$V_{th} = V$$


$$5V = 26$$

$$V = \frac{26}{5}$$


$$V = 5.2V$$

⇒ Solution

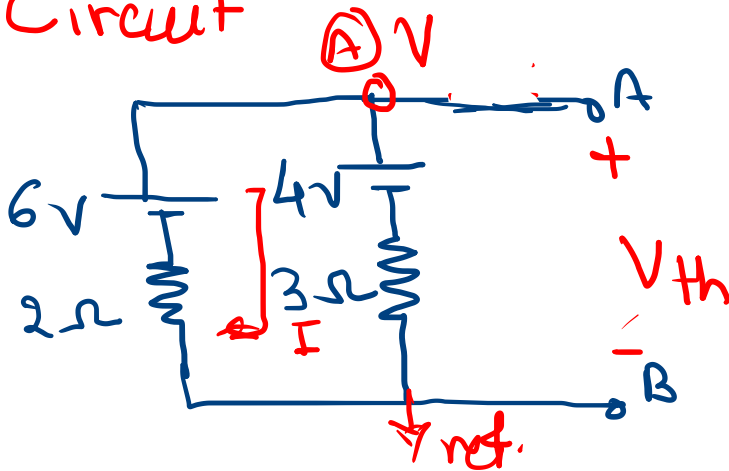① Remove  $R_L = 10\Omega$  from the circuit



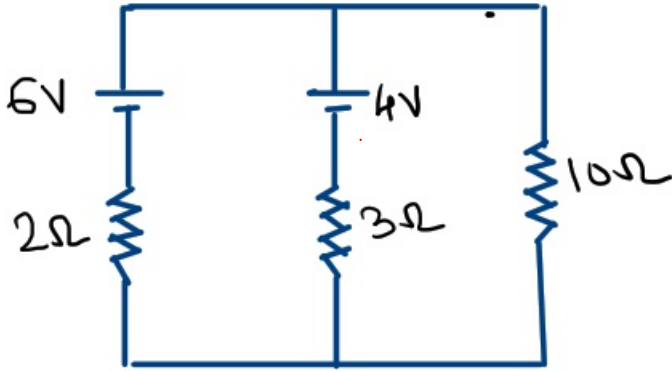
**Example:1 Find current through 10 Ohm resistor using Thevenin's Theorem**



$$R_{th} = (2 || 3)$$

$$R_{th} = \frac{6}{5} = 1.2 \Omega$$

④ Draw Thevenin's Equivalent Circuit.

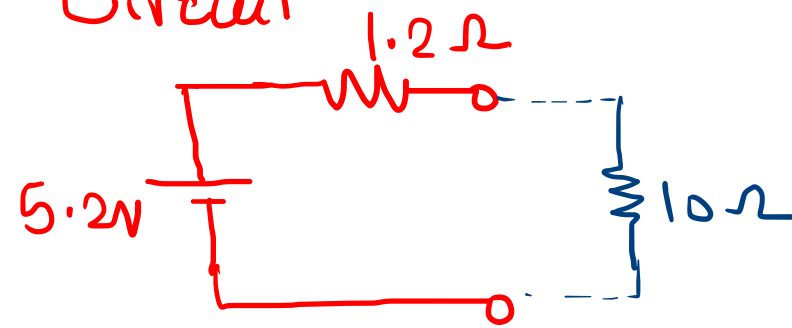


⑤ Connect load & find Current


$$I_{10\Omega} = \frac{5.2}{(1.2 + 10)} = \frac{5.2}{11.2} = 0.46 A \downarrow$$

⇒ Solution

③ find  $R_{th}$

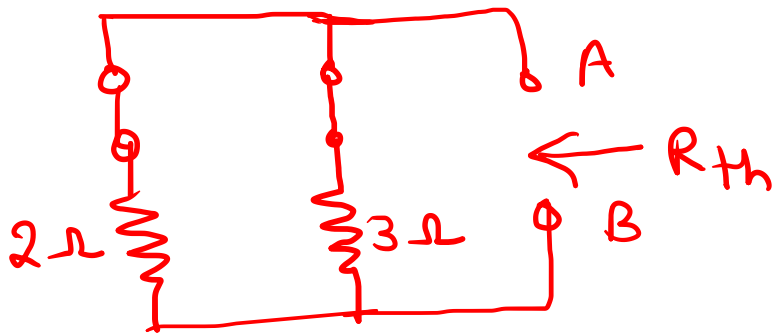
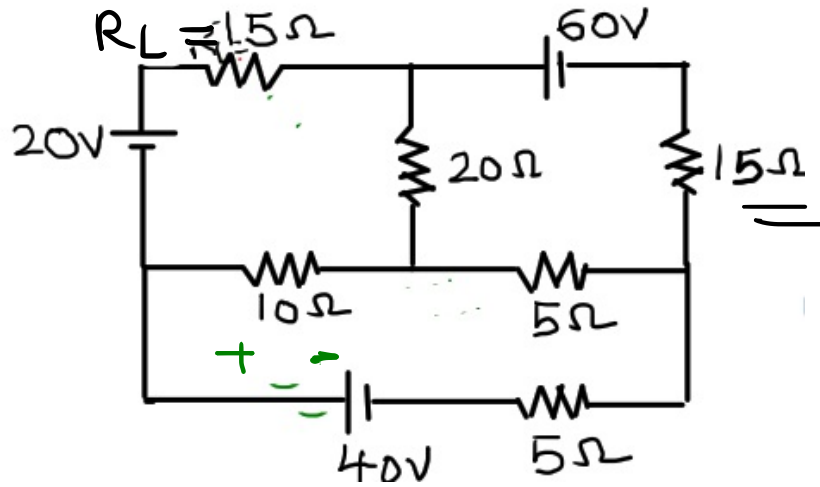
### Ex:3 Find current through $R_L=15\ \Omega$ resistor using Thevenin's Theorem



② Find  $V_{th}$

$$V_{th} - 20 - V_{10\Omega} - V_{20\Omega} = 0$$

$$V_{th} = 20 + V_{10\Omega} + V_{20\Omega}$$

using mesh Analysis

KVL to mesh (I)

$$-10I_1 - 5(I_1 - I_2) - 5I_1 + 40 = 0$$

$$-20I_1 + 5I_2 = -40$$

$$20I_1 - 5I_2 = 40 \quad \text{--- (1)}$$

KVL to mesh (II)

$$-60 - 15I_2 - 5(I_2 - I_1) - 20I_2 = 0$$

$$5I_1 - 40I_2 = 60 \quad \text{--- (2)}$$

Solving (1) & (2)  $I_1 = 1.68\ \text{A}$


$$I_2 = -1.29\ \text{A}$$

$$V_{th} = 20 + (10 \times 1.68) + (20 \times -1.29)$$



$$V_{th} = 20 + 16.8 - 25.8 = 11\ \text{V}$$

⇒ Solution

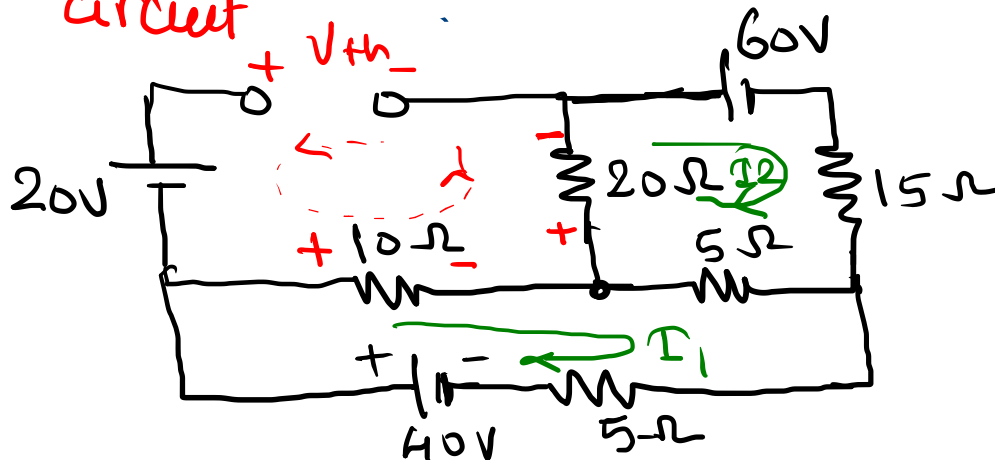① Remove  $R_L=15\ \Omega$  from the circuit



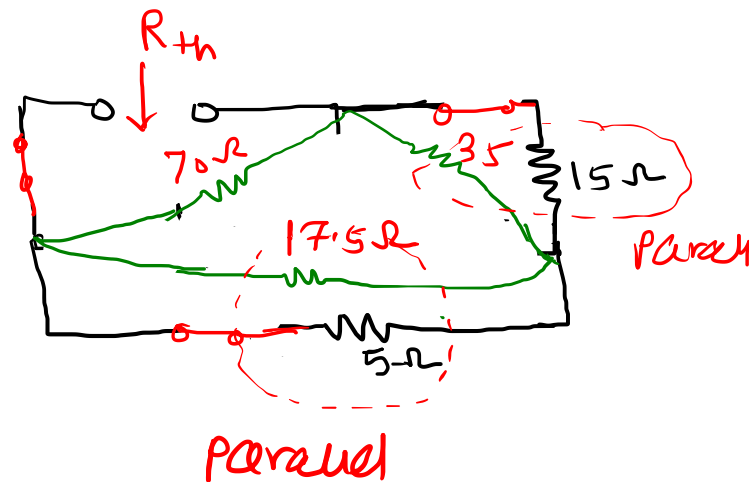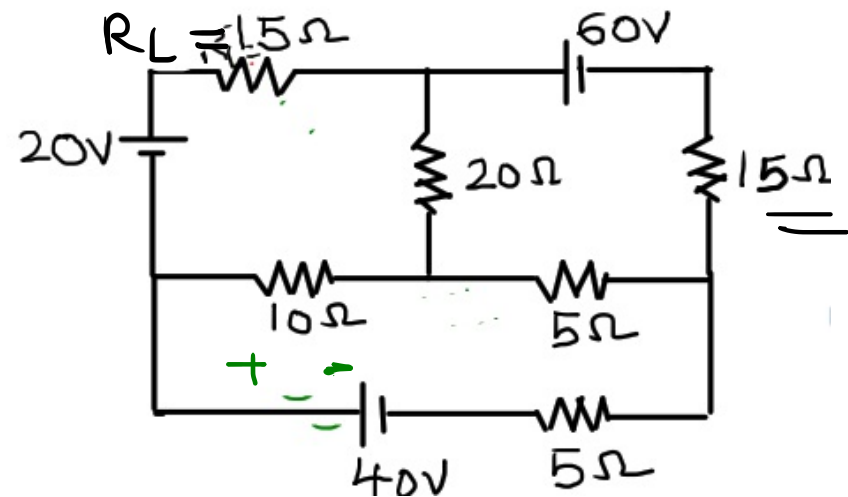
### Ex:3 Find current through $R_L=15\ \Omega$ resistor using Thevenin's Theorem



⇒ (3) Find  $R_{th}$ ...


$$35 \parallel 15 = \frac{35 \times 15}{35 + 15} = 10.5\ \Omega$$
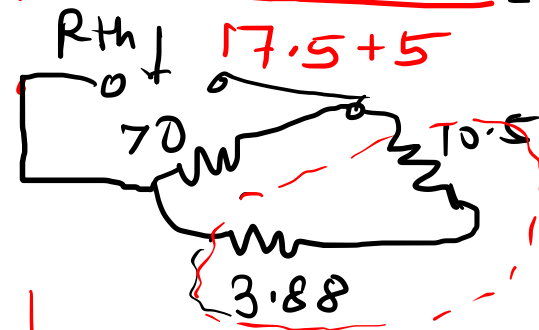
$$17.5 \parallel 5 = \frac{17.5 \times 5}{17.5 + 5} = 3.88$$



$$R_{th} = 70 \parallel (10.5 + 3.88)$$
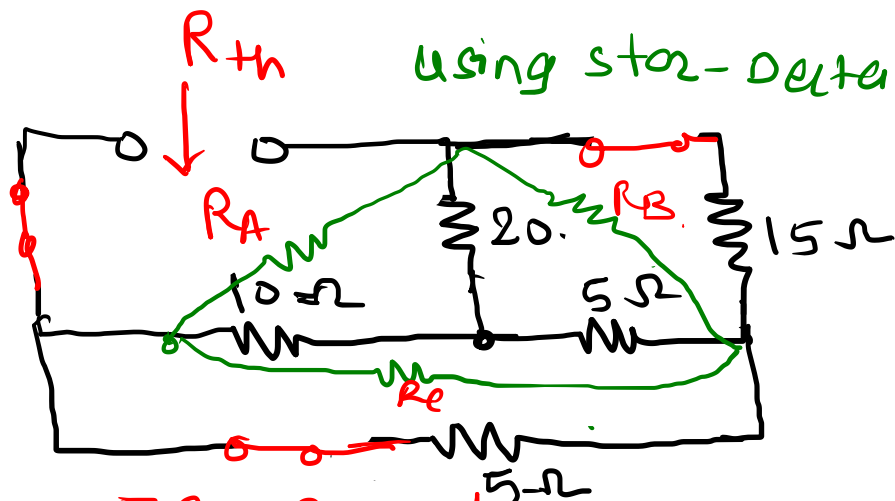
$$R_{th} = 70 \parallel 14.38 = 11.9\ \Omega$$




$$R_A = \frac{\sum R}{5} = \frac{35}{5} = 7$$

$$R_B = \frac{\sum R}{10} = \frac{35}{10} = 3.5$$


$$R_C = \frac{\sum R}{20} = \frac{35}{20} = 1.75$$

$$\sum R = 20 \times 5 + 5 \times 10 + 10 \times 20 = 100 + 50 + 200 = 350$$
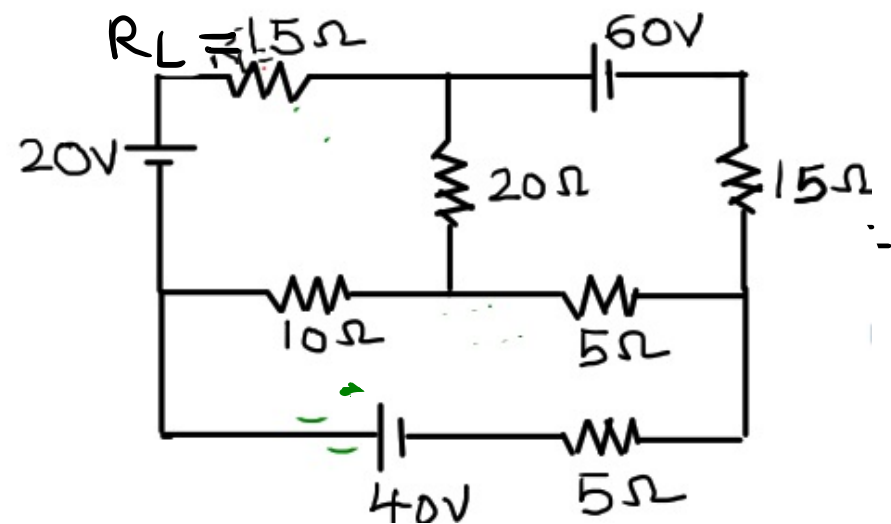
### Ex:3 Find current through $R_L=15\ \Omega$ resistor using Thevenin's Theorem




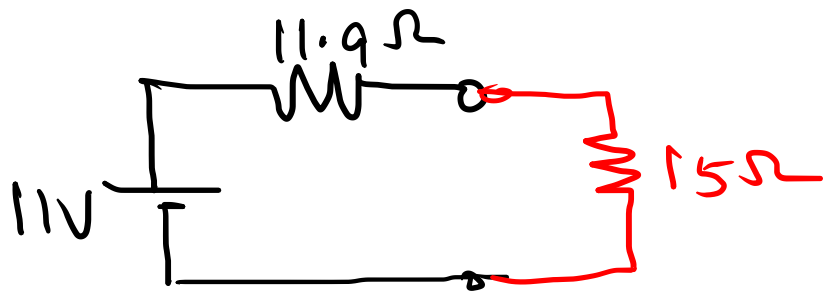⇒ (4) Draw thevenin's Equivalent Circuit & Connect load.




$$I_{15\ \Omega} = \frac{11}{11.9 + 15} = \frac{11}{26.9} = 0.4\text{A} \downarrow$$

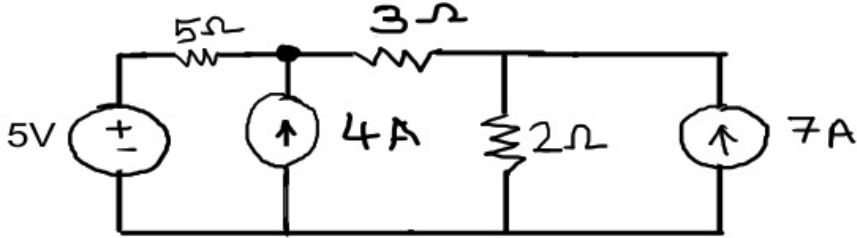**Ex:3 Find voltage across 2 Ohm resistor using Thevenin's Theorem**



⇒ Solution:

① Remove load resistance

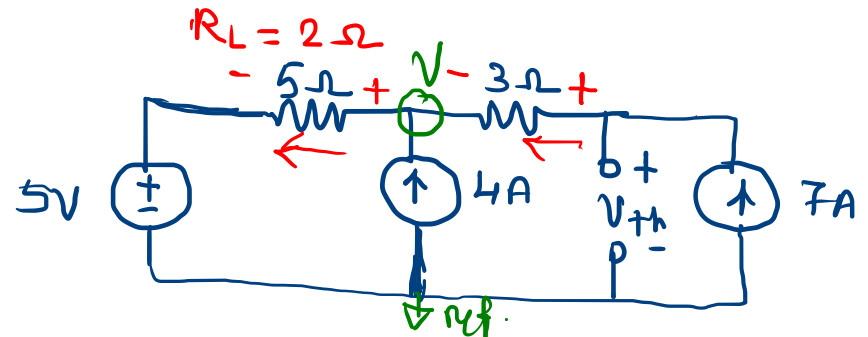

$V_{th} = \text{Voltage across } 7A \text{ source}$

OR

$$V_{th} = \text{Voltage across } 3\Omega \text{ \& } 4A = V_{3\Omega} + V_{4A}$$

OR

$$V_{th} = (V_{3\Omega} + V_{5\Omega} + 5V)$$

$$\left\{ \begin{aligned} V_{3\Omega} &= I_{3\Omega} \times 3 = 7 \times 3 = 21V \\ V_{5\Omega} &= I_{5\Omega} \times 5 = (4+7) \times 5 = 55V \\ V_{th} &= (21 + 55 + 5) = 81V \end{aligned} \right.$$

OR

Using Nodal Analysis

KU at node

$$\frac{V-5}{5} = 4+7 = 11$$

$$V-5 = 55 \quad \therefore V = 60V$$


$$V_{th} = V_{3\Omega} + V$$

$$V_{th} = 21 + 60 = 81V$$

81  
8  
16.7




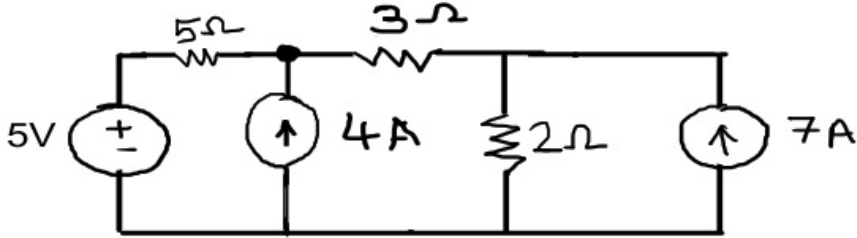**Ex:3 Find voltage across 2 Ohm resistor using Thevenin's Theorem**




⇒ Solution.

③ To find  $R_{Th}$

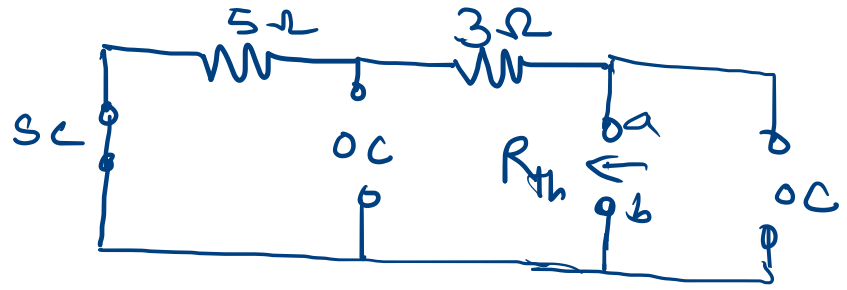

$$R_{Th} = (5 + 3) = 8\Omega$$

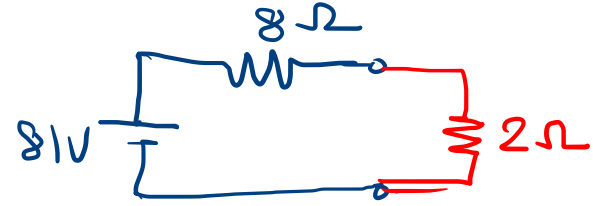④ Draw equivalent circuit & connect load.



$$V_{2\Omega} = \frac{2 \times 81}{8 + 2}$$

$$V_{2\Omega} = \frac{81}{5}$$


$$V_{2\Omega} = 16.2V$$

81  
8  
16.2

# Norton's Theorem

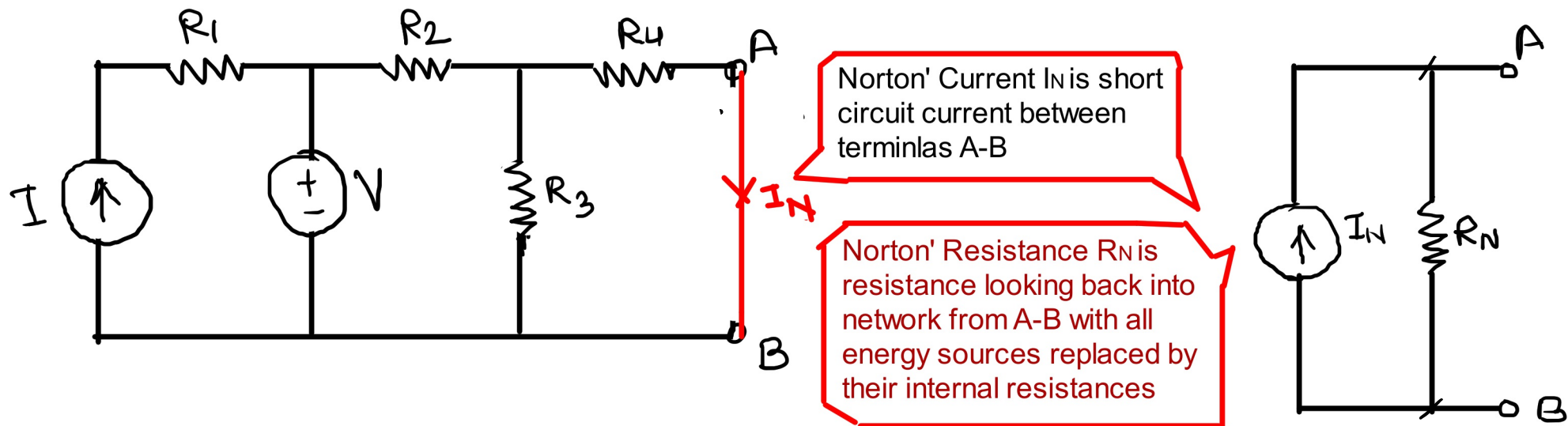
## Statement:

Any linear, active bilateral network can be replaced by a current source ( $I_N$ ) in parallel with a resistance ( $R_N$ ) where  $I_N$  is the short-circuit current (i.e. current through the two terminals when  $R_L$  is removed) and  $R_N$  is the internal resistance of the network as viewed back into the open-circuited network from terminals A and B with all energy sources replaced by their internal resistance (if any) and current sources by infinite resistance.




# Norton's Theorem

Given Network

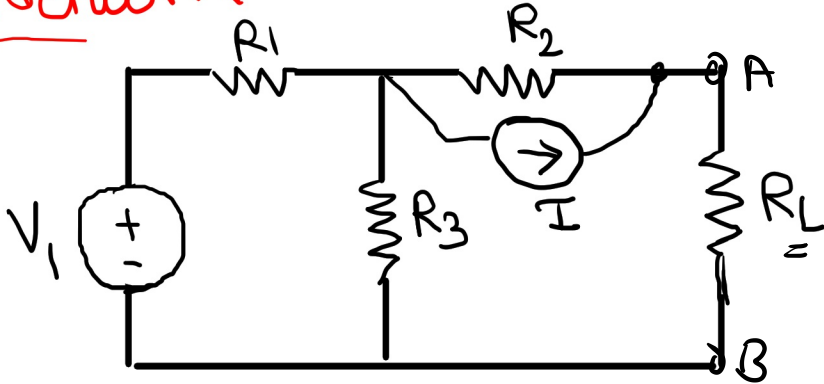


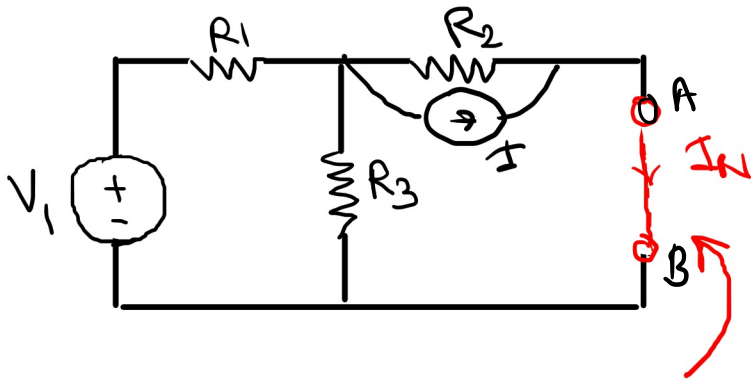1. Remove the load  $R_L$  from the circuit




2. Find  $I_N$  i.e. the short circuit current between the terminals (A-B) from where the load is removed, using any suitable method (mesh, nodal, source transformation etc..)

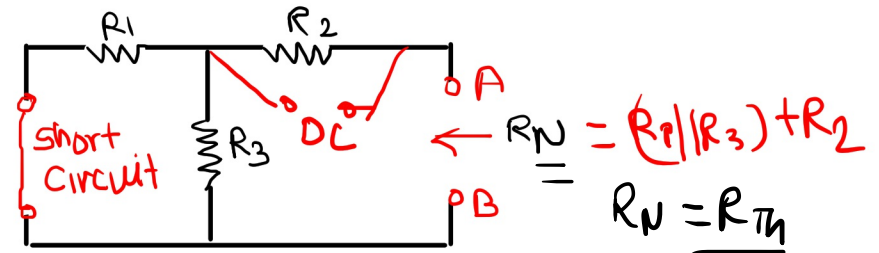
3. Find  $R_N$  i.e. resistance looking back into the network from the terminals (A-B) from where the load is removed with energy sources replaced by their internal resistances.



4. Draw Norton's equivalent circuit

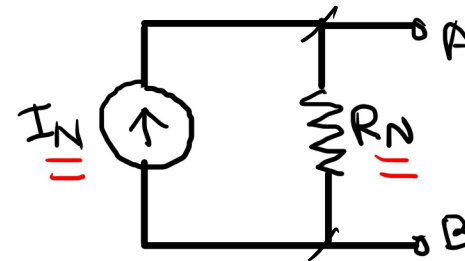

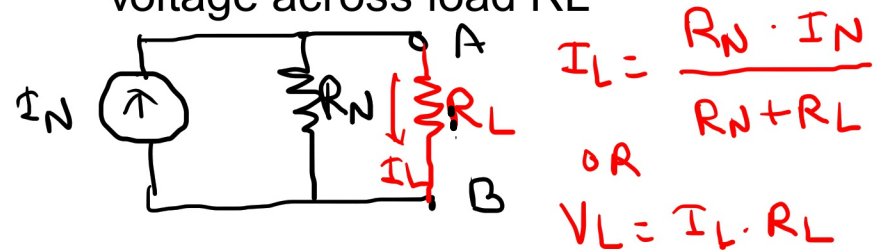5. Connect the load  $R_L$  and find current/voltage across load  $R_L$




$$I_L = \frac{R_N \cdot I_N}{R_N + R_L}$$

OR

$$V_L = I_L \cdot R_L$$


# Relation between Thevenin and Norton Equivalent Circuit

Thevenin's Equivalent Circuit

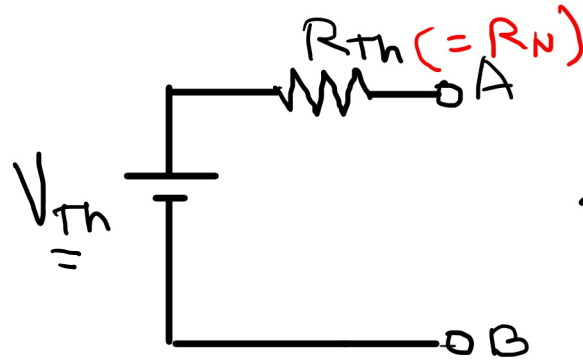

$$V_{Th} = I_N \cdot R_N$$

Norton's Equivalent Circuit

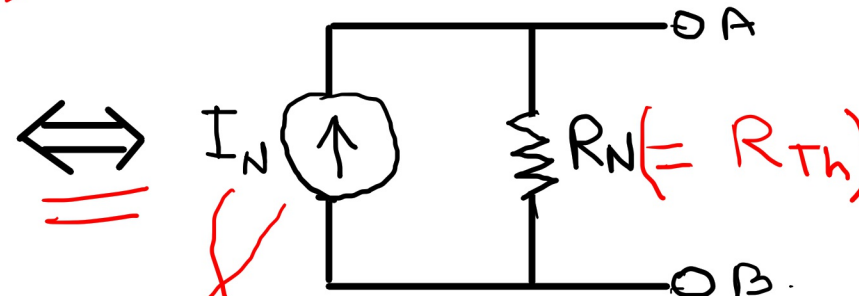


$$I_N = \frac{V_{Th}}{R_{Th}}$$

Norton's equivalent circuit can be obtained by applying source transformation to Thevenin's equivalent circuit.

Also

Thevenin's equivalent circuit can be obtained by applying source transformation to Norton's equivalent circuit.

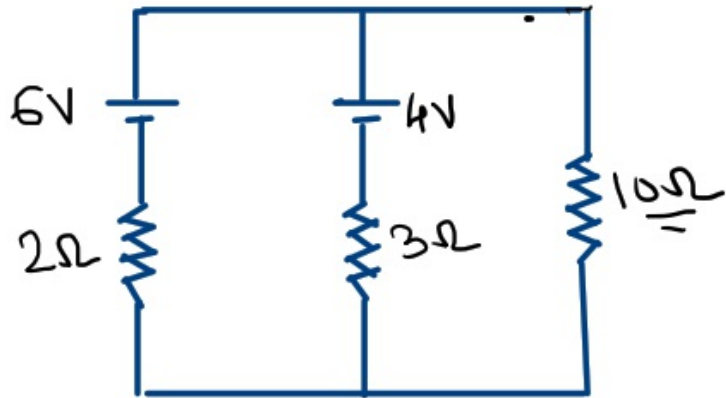① Find current flowing through  $10\Omega$  resistor using Norton's theorem.



⇒ using mesh Analysis

KVL to mesh (I)

$$-2I_1 + 6 - 4 - 3(I_1 - I_2) = 0$$

$$-5I_1 + 3I_2 = -2 \quad \text{--- (i)}$$

KVL to mesh (II)

$$-3(I_2 - I_1) + 4 = 0$$

$$3I_1 - 3I_2 = -4 \quad \text{--- (ii)}$$


Solving (i) & (ii)

$$I_1 = 3A \quad I_2 = 4.33A$$

$$I_N = I_2 = 4.33A$$


⇒ Solution.

① Remove load  $R_L = 10\Omega$

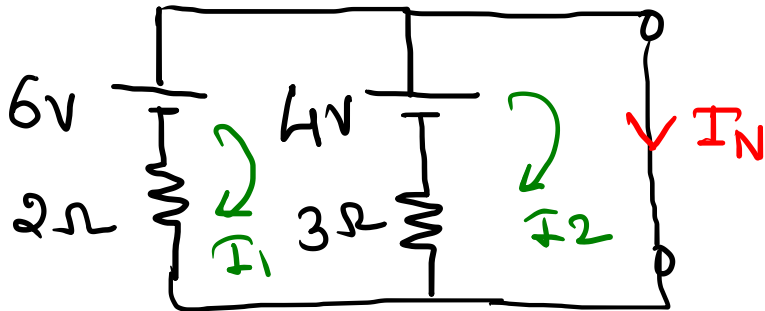


② Find short circuit current ( $I_N$ )

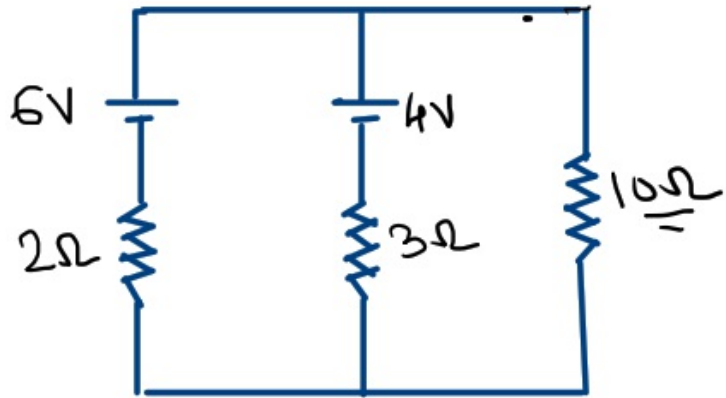① Find current flowing through  $10\Omega$  resistor using Norton's theorem.




③ to find  $R_N$

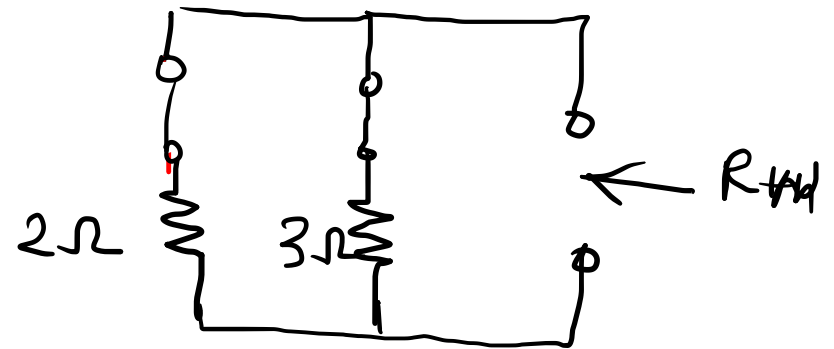

$$R_N = 2 \parallel 3 = \frac{6}{5} = 1.2\Omega$$


④ Draw Norton's Equivalent circuit

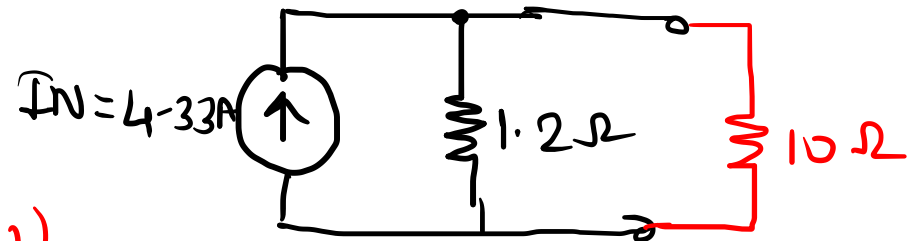

$$I_{10\Omega} = \frac{1.2 \times 4.33}{1.2 + 10} = 0.46A$$

⇒ Solution.

① Remove load  $R_L = 10\Omega$


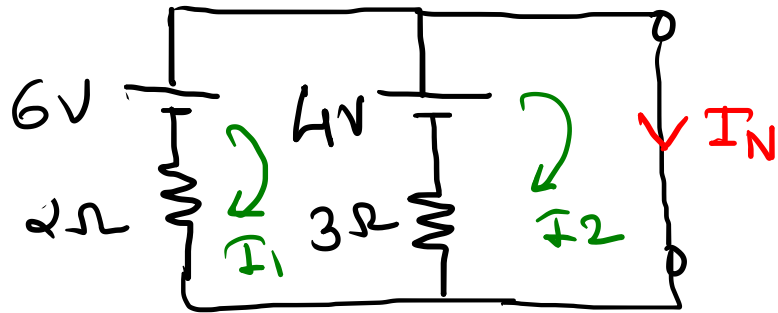


② Find short circuit current ( $I_N$ )

⇒ Thevenine Eq.ckt.



$$4.33 \times 1.2 = 5.19V$$

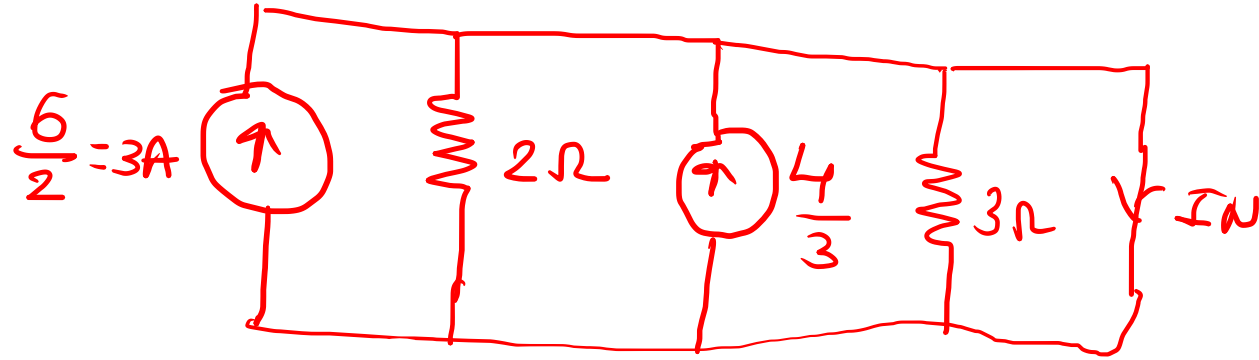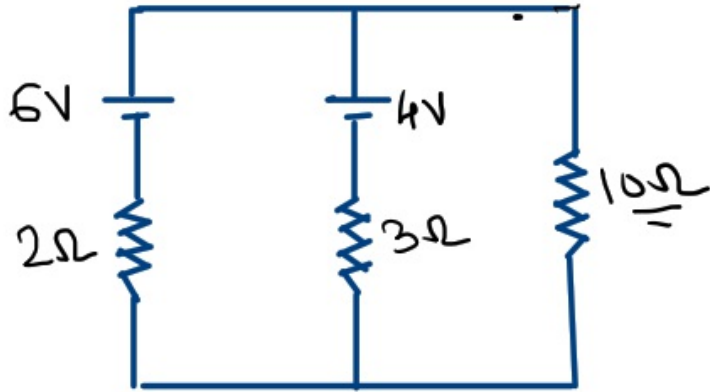① Find current flowing through  $10\Omega$  resistor using Norton's theorem.




⇒ Solution.

① Remove load  $R_L = 10\Omega$

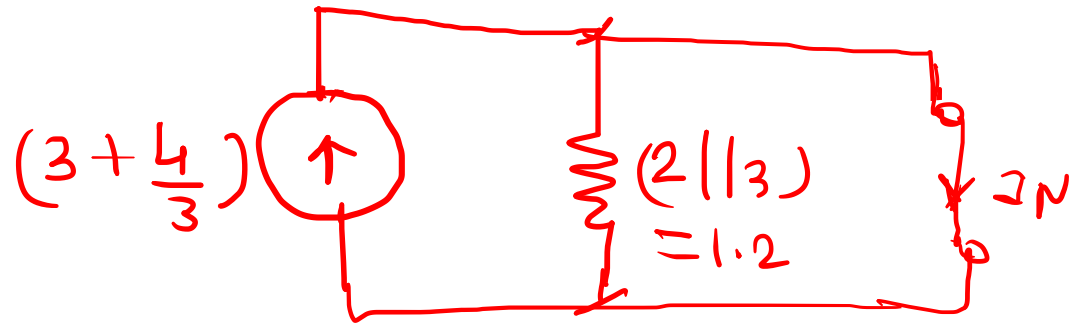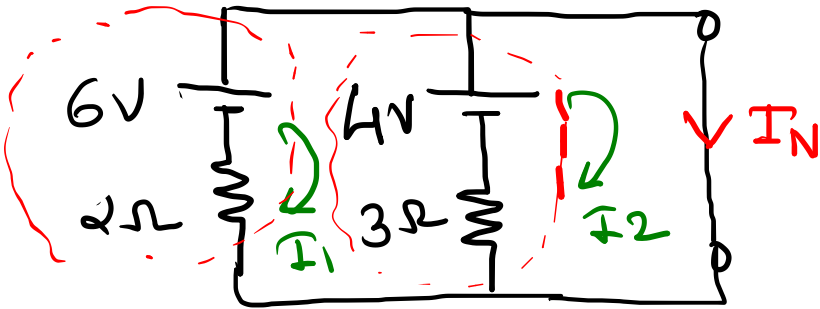


② Find short circuit current ( $I_N$ )




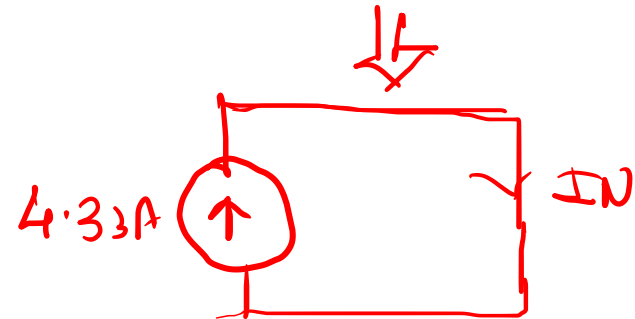


$$I_N = 4.33\text{A}$$

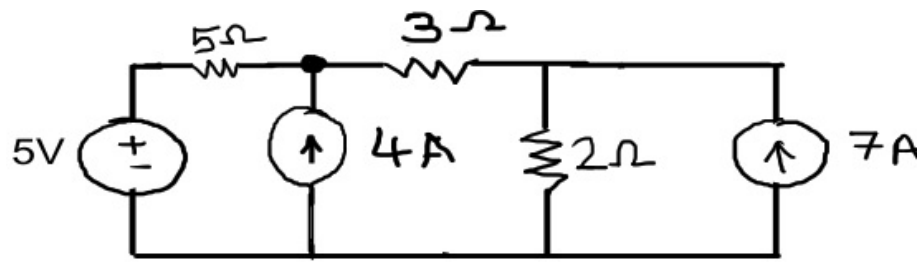Ex. ② Find Current in  $2\Omega$  resistor using Norton's theorem.




⇒ Source transformation

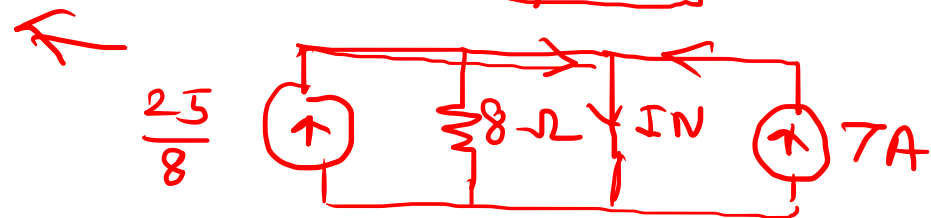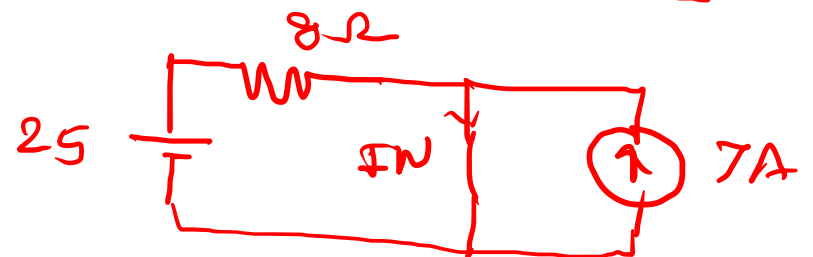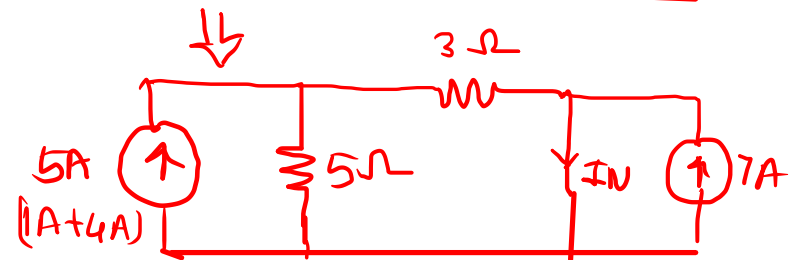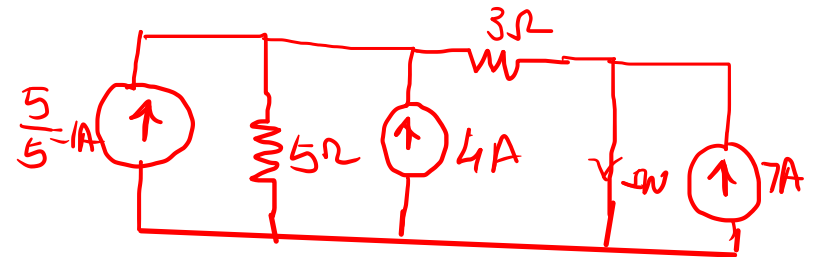

⇒ Solution

① Remove  $R_L = 2\Omega$ .

② Short circuit & find  $I_N$ .

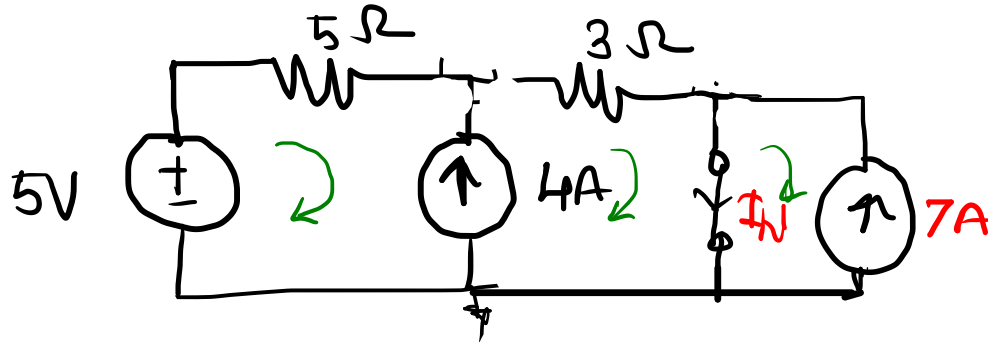


Using KCL

$$I_N = \frac{25}{8} + 7 = 10.1A$$




Ex. ② Find Current in  $2\Omega$

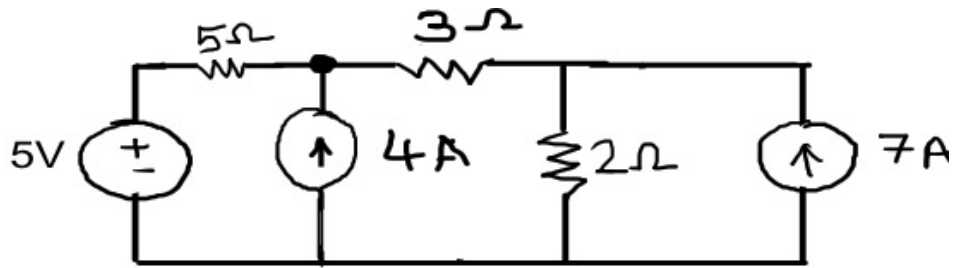


⇒ Solution

① Remove  $R_L = 2\Omega$ .


② Short circuit & find  $I_N$ .

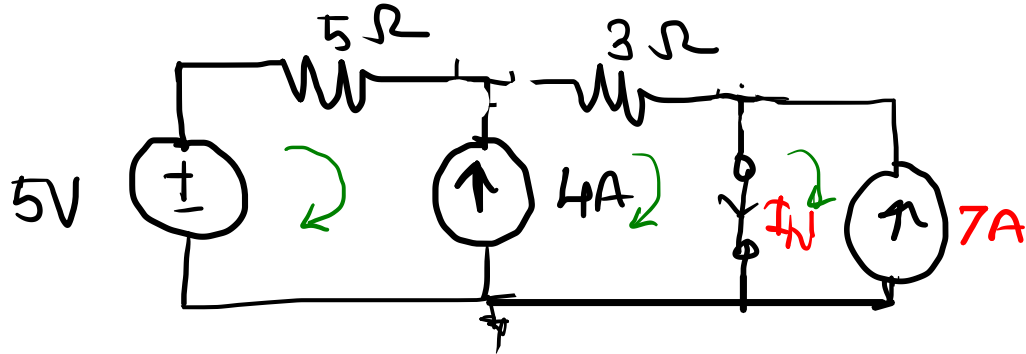

⇒ Thevenin's Eq. Calc.

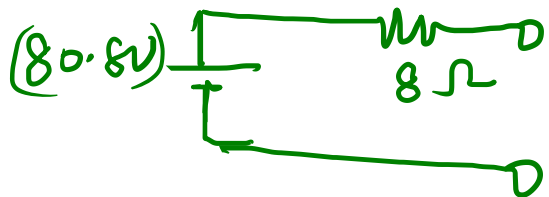


③ find  $R_N$ .

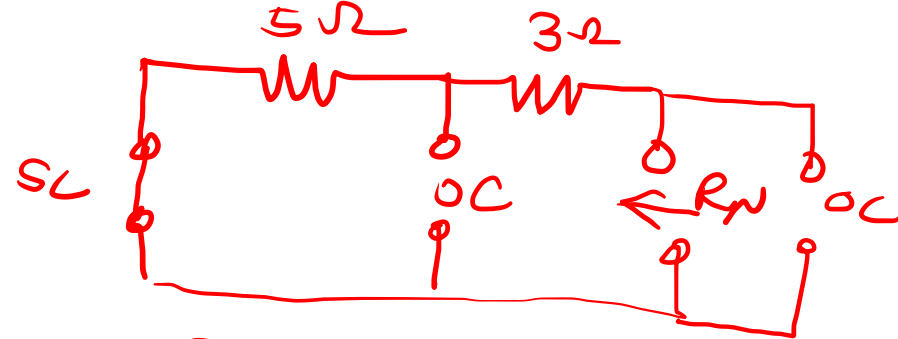

$$R_N = 5 + 3 = 8\Omega$$

④ Norton's Equivalent

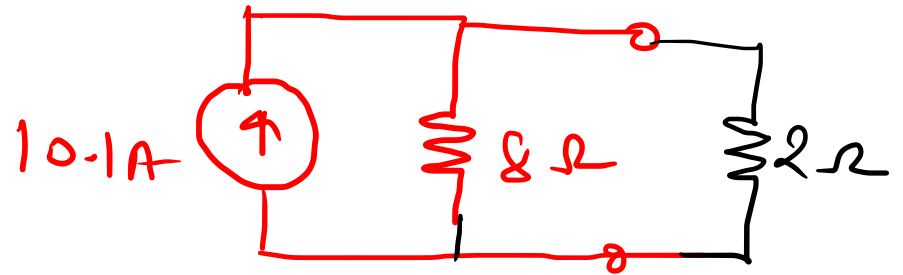


$$I_{2\Omega} = \frac{8 \times 10.1}{8 + 2} = 8.1\text{A}$$

$$V_{2\Omega} = 8.1 \times 2 = 16.2\text{V}$$


# Norton's Theorem

Q.1 Find current flowing through 10 Ohm resistance using Norton's theorem

$$I_{10} = 0.46A$$

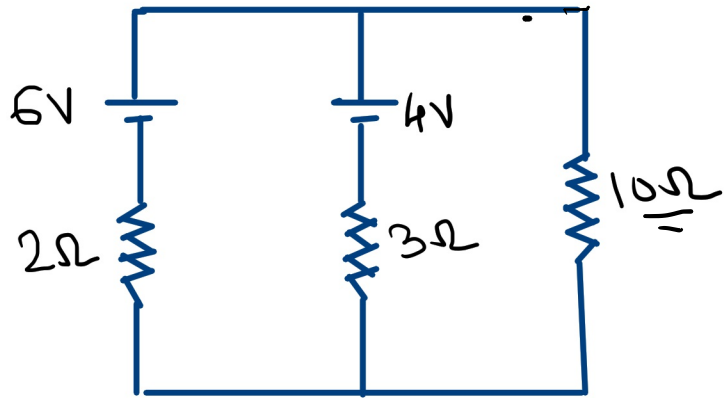


① Remove load  $R_L = 10\Omega$

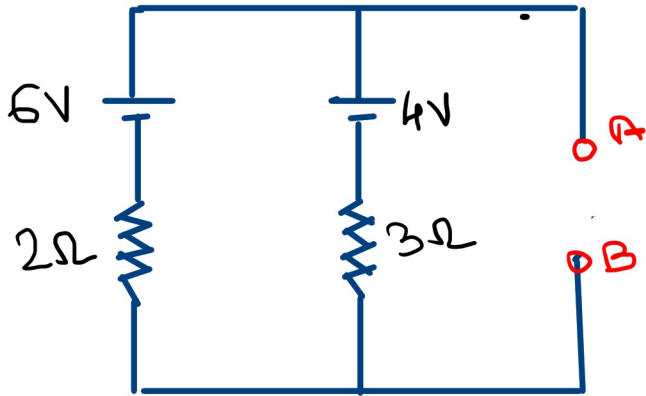

② Short circuit A & B & find

$$I_N = I_{sc}$$

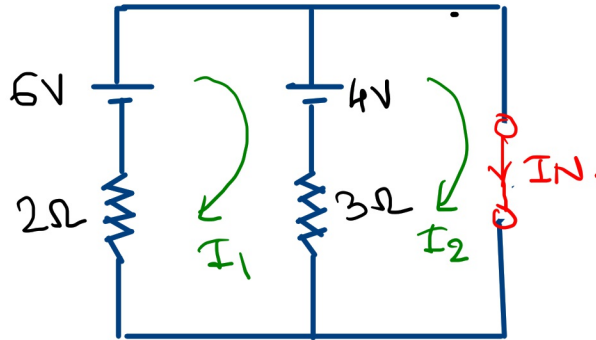

$$I_N = I_2$$

→ Using mesh Analysis.

Mesh ①

$$-2I_1 + 6 - 4 - 3(I_1 - I_2) = 0$$

$$5I_1 - 3I_2 = 2 \quad \text{--- (i)}$$

→ mesh ②

$$-3(I_2 - I_1) + 4 = 0$$

$$3I_1 - 3I_2 = -4 \quad \text{--- (ii)}$$


Solving (i) & (ii)  $I_1 = 3A$        $I_2 = 4.33A$

$$I_N = I_2 = 4.33A$$

# Norton's Theorem


Q.1 .....

③ Find  $R_N = R_{eq}$ .

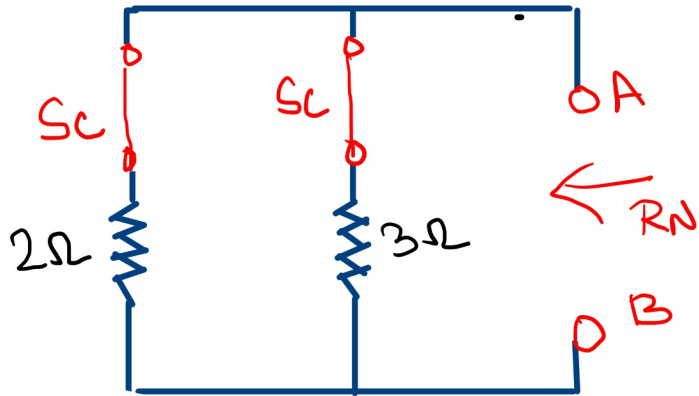


$$R_N = 2 \parallel 3 = \frac{6}{5} = 1.2 \Omega$$

④ Draw Norton's Equivalent Circuit

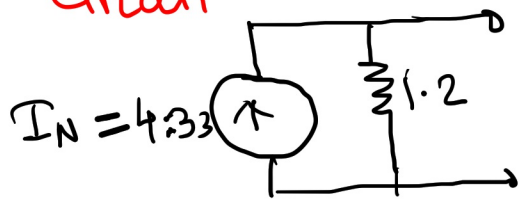


⇒

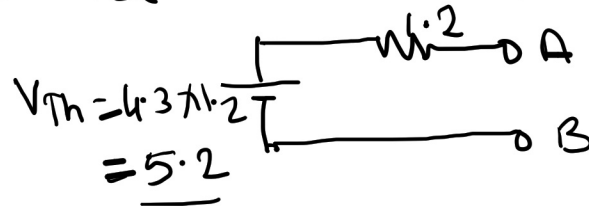source transformation (Thevenin's Equivalent)



⑤ Connect  $R_L = 10 \Omega$

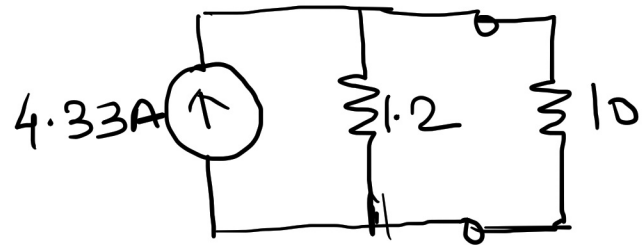


using current division formula

$$I_{10\Omega} = \frac{1.2 \times 4.33}{1.2 + 10}$$


$$I_{10\Omega} = 0.46A$$

$$I_{10} = 0.46A$$




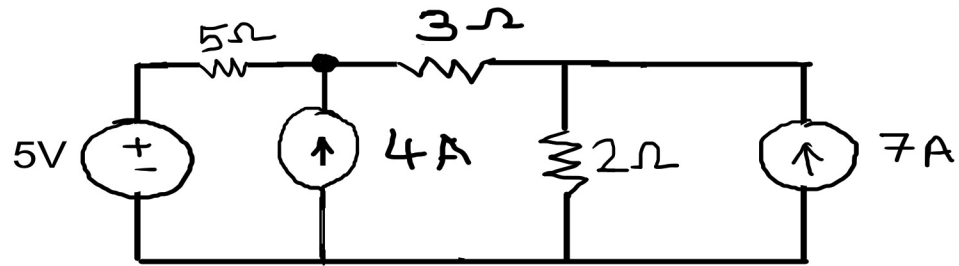
Example:- 2. Find voltage across 2 Ohm resistor using Norton's Theorem



① Remove  $R_L = 2\Omega$  & find  $I_N$

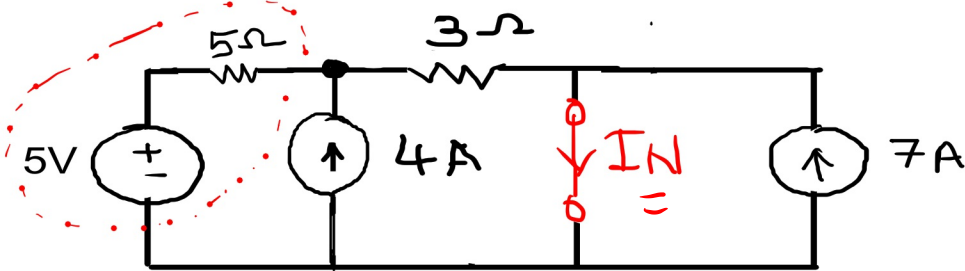

using source transformation

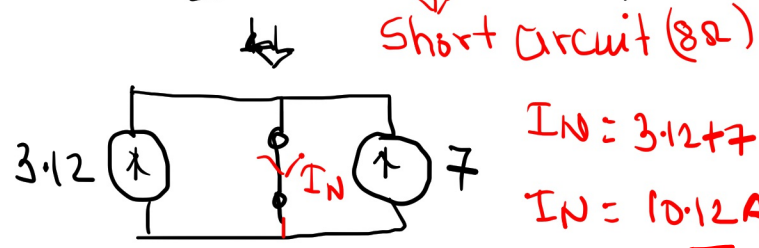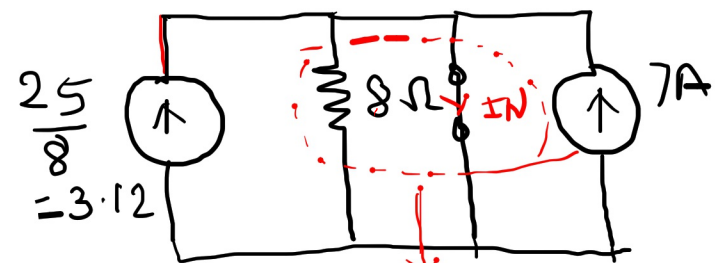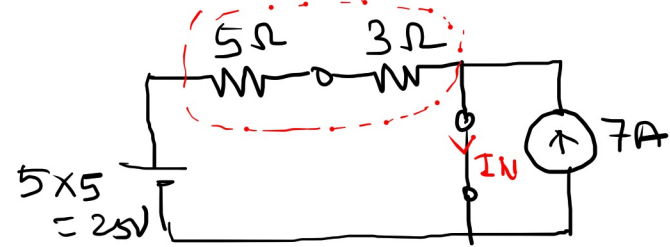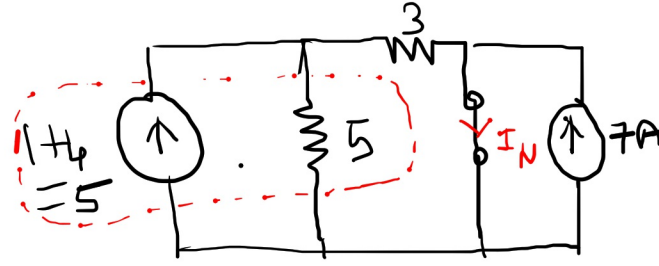

$$I_N = 3.12 + 7$$

$$I_N = 10.12 \text{ A}$$

$$I_N = \frac{8}{8}$$

$$R_N = 8\Omega$$

$$I_{2\Omega} = \frac{8}{10}$$


$$V_{2\Omega} = 16.2$$

Redundant

$$\frac{8 \times 0}{8 + 0} = 0$$


Example:- 2. ....

③ Find  $R_N$

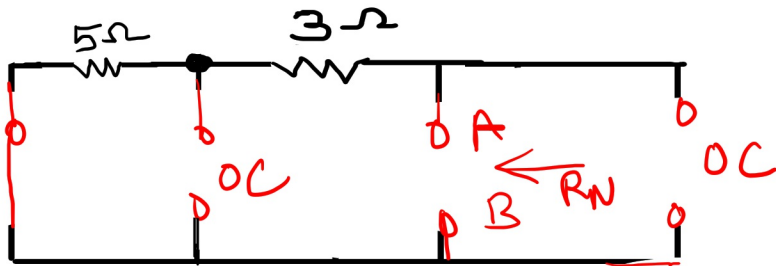

$$R_N = 5 + 3 = 8 \Omega$$

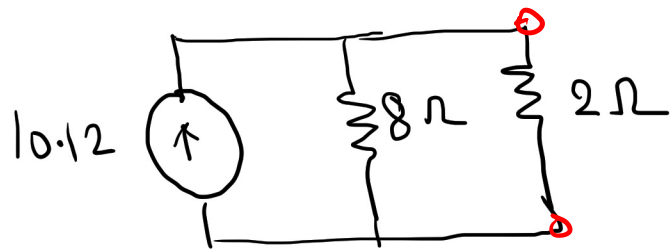④ Draw Norton's Equivalent circuit & Connect load.



Using current division

$$I_{2\Omega} = \frac{10.12 \times 8}{10}$$

$$I_{2\Omega} = 8.09 \text{ A}$$

$$V_{2\Omega} = I_{2\Omega} \times 2$$

$$= 8.09 \times 2$$

$$\underline{V_{2\Omega} = 16.2 \text{ V}}$$


$$I_N = \frac{81}{8}$$

$$R_N = 8 \Omega$$


$$I_{2\Omega} = \frac{81}{10}$$

$$V_{2\Omega} = 16.2$$

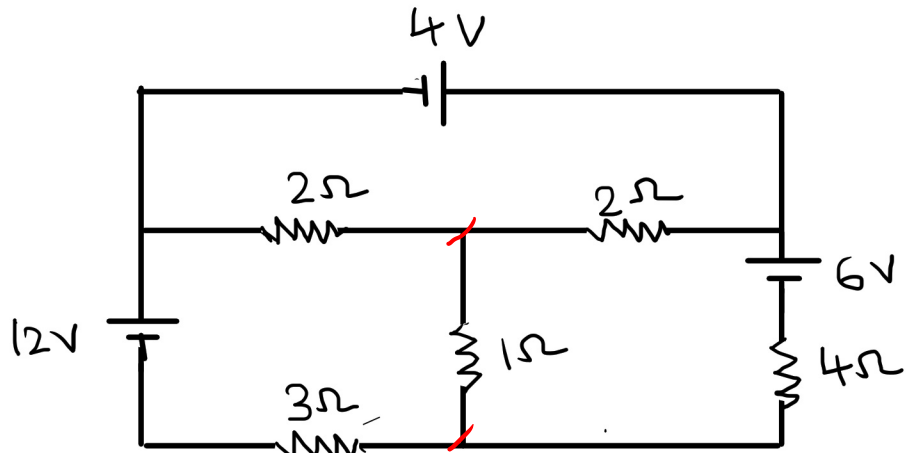Example:- 3. Find current flowing through 1 Ohm resistor, using Norton's Theorem.



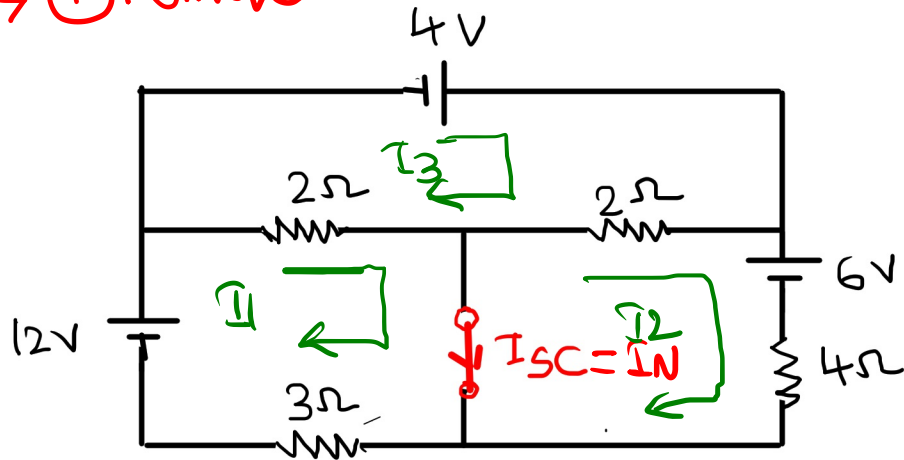⇒ ① Remove load & short circuit & find  $I_N$



using mesh Analysis

$$I_N = (I_1 - I_2) \downarrow$$

KVL to mesh ①

$$12 - 2(I_1 - I_3) - 3I_1 = 0$$

$$5I_1 - 2I_3 = 12 \quad \text{--- ①}$$

KVL to mesh ②

$$-2(I_2 - I_3) - 6 - 4(I_2) = 0$$

$$6I_2 - 2I_3 = -6 \quad \text{--- ②}$$

KVL to mesh ③

$$4 - 2(I_3 - I_2) - 2(I_3 - I_1) = 0$$



$$2I_1 + 2I_2 - 4I_3 = -4 \quad \text{--- ③}$$

Solving ①, ② & ③



$$I_1 = 3.47A, \quad I_2 = -0.1A, \quad I_3 = 2.68A$$

$$I_N = I_1 - I_2 = 3.47 - (-0.1) = 3.57A \downarrow$$

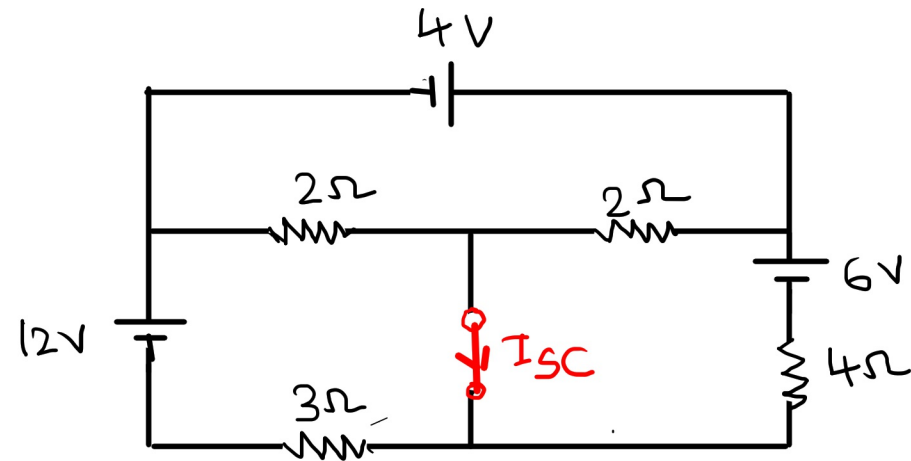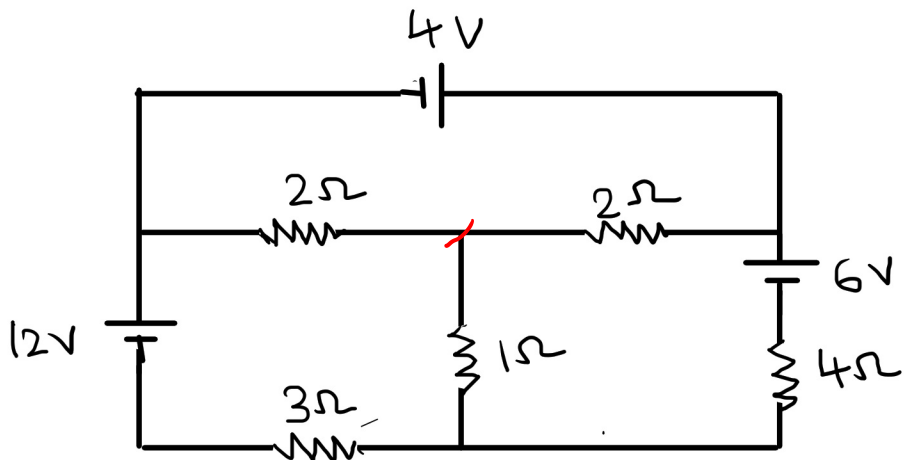Example:- 3. Find current flowing through 1 Ohm resistor, using Norton's Theorem.




⇒ To find  $R_N = R_{Th}$

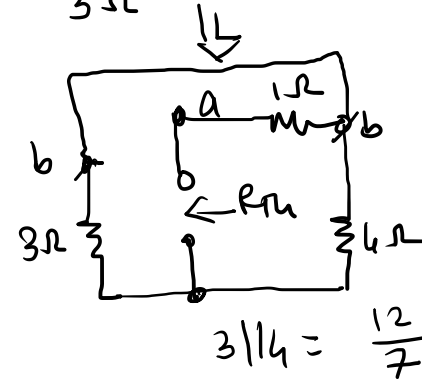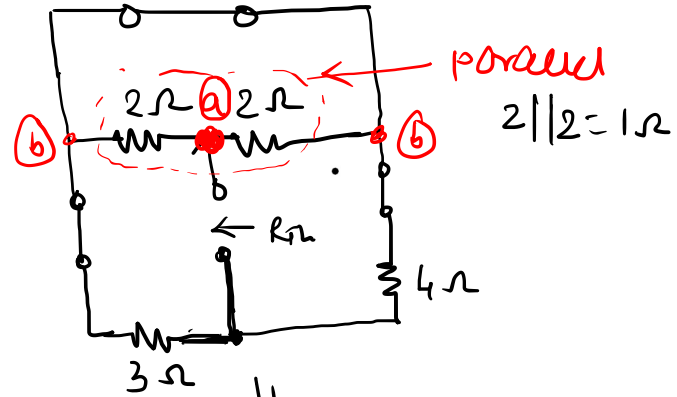

$$R_N = \frac{12}{7} + 1 = 2.71 \Omega$$

⇒ Norton's Equivalent Circuit

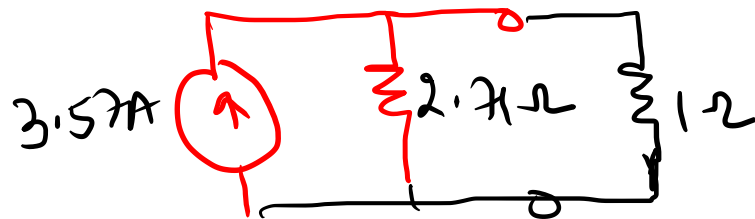

Current division Rule

$$I_{1\Omega} = \frac{2.71 \times 3.57}{2.71 + 1} = 2.6A$$